

NANO PROCESSOR DESIGN COMPETITION**LAB REPORT**

- **A.A.A. Jasmin - 200238N**
- **K.G.T.R. Kumaratunga - 200327L**
- **K.V.R. Kurukulasooriya - 200332X**
- **G.S.D. Kuruppu - 200333C**
- **G.M.P. Silva - 200605M**

TASK ASSIGNED:

1. Design and develop a 4-bit arithmetic unit that can add and subtract signed integers
2. Modify 4-bit RCA developed to a 3-bit adder
3. Design and develop 3-bit program counter which needs to reset to 0 when required
4. Design and develop k -way b -bit multiplexers or tri-state busses
5. Design and develop register bank with the required functionality
6. Extend ROM based LUT developed to store the assembly program to run
7. Decode instructions to activate necessary components on the processor
8. Connect all built and modified components to the design the nano processor.
9. Write a constraint file to connect inputs and outputs.
10. Verify their functionality via simulation and on the development board

ASSEMBLY PROGRAM AND MACHINE CODE REPRESENTATION

MOVI R1,1	10 001 000 0001
MOVI R2,2	10 010 000 0010
MOVI R7,3	10 111 000 0011
ADD R7,R2	00 111 010 0000
ADD R7,R1	00 111 001 0000
JZR R0,7	11 000 0000 111
ADD R0,R0	00 000 000 0000
JZR R0,5	11 000 0000 101

Synthesis Report Summary

1. Slice Logic

Site Type	Used	Fixed	Available	Util%
Slice LUTs*	52	0	20800	0.25
LUT as Logic	52	0	20800	0.25
LUT as Memory	0	0	9600	0.00
Slice Registers	53	0	41600	0.13
Register as Flip Flop	53	0	41600	0.13
Register as Latch	0	0	41600	0.00
F7 Muxes	0	0	16300	0.00
F8 Muxes	0	0	8150	0.00

7. Primitives

Ref Name	Used	Functional Category
FDRE	37	Flop & Latch
LUT5	25	LUT
OBUF	17	IO
LUT4	17	LUT
FDCE	16	Flop & Latch
LUT6	13	LUT
CARRY4	8	CarryLogic
LUT3	5	LUT
IBUF	2	IO
LUT2	1	LUT
LUT1	1	LUT
BUFG	1	Clock

How we achieved the above results

- Instead of using previously built components, we built 3 to 8 decoders, multiplexers, and 4 bit adder subtractors from ground up that resulted in 52 slice LUTs and 53 slice registers as flip flops.

VHDL FILES

SLOW CLOCK

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if
instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC := '1');
end Slow_Clk;
architecture Behavioral of Slow_Clk is
    signal count : integer := 1;
    signal clk_status : std_logic := '0';
begin
    process (Clk_in) begin
        if (rising_edge(Clk_in)) then
            count <= count + 1;
            if (count = 1) then
                -- if (count = 100000000) then
                    clk_status <= not clk_status;
                    Clk_out <= clk_status;
                    count <= 1;
                end if;
            end if;
        end process;
    end process;
```

INSTRUCTION DECODER

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Decoder is
    Port ( Ins : in STD_LOGIC_VECTOR (11 downto 0);
          RegJmp : in STD_LOGIC_VECTOR (3 downto 0);
          RegEn : out STD_LOGIC_VECTOR (2 downto 0);
          LoadSel : out STD_LOGIC;
          ImVal : out STD_LOGIC_VECTOR (3 downto 0);
          RegSel1 : out STD_LOGIC_VECTOR (2 downto 0);
          RegSel2 : out STD_LOGIC_VECTOR (2 downto 0);
          AddSubSel : out STD_LOGIC;
          Jmp : out STD_LOGIC;
          AddressJmp : out STD_LOGIC_VECTOR (2 downto 0));
end Instruction_Decoder;

architecture Behavioral of Instruction_Decoder is
begin
    RegEn <= Ins(9 downto 7);
    LoadSel <= Ins(11) AND NOT(Ins(10));
    ImVal <= Ins(3 downto 0);
    RegSel1 <= Ins(9 downto 7);
    RegSel2 <= Ins(6 downto 4);
    AddSubSel <= NOT(Ins(11)) AND Ins(10);
    AddressJmp <= Ins(2 downto 0);
    Jmp <= Ins(11) AND Ins(10) AND NOT (RegJmp(3) OR
    RegJmp(2) OR RegJmp(1) OR RegJmp(0));

end Behavioral;
```

REGISTER BANK

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Reg_Bank is

    Port ( En : in STD_LOGIC_VECTOR (2 downto 0);

          Clk : in STD_LOGIC;

          Res : in STD_LOGIC;

          D : in STD_LOGIC_VECTOR (3 downto 0);

          Q0 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";

          Q1 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";

          Q2 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";

          Q3 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";

          Q4 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";

          Q5 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";

          Q6 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";

          Q7 : out STD_LOGIC_VECTOR (3 downto 0) := "0000");

end Reg_Bank;

architecture Behavioral of Reg_Bank is

    Component Reg_4

        Port ( En : in STD_LOGIC;

              Clk : in STD_LOGIC;

              D : in STD_LOGIC_VECTOR (3 downto 0);

              Res : in STD_LOGIC;

              Q : out STD_LOGIC_VECTOR (3 downto 0) := "0000");

    End Component;

    Component Decoder_3_to_8

        Port ( I : in STD_LOGIC_VECTOR (2 downto 0);

              Y0 : out STD_LOGIC;

              Y1 : out STD_LOGIC;

              Y2 : out STD_LOGIC;

              Y3 : out STD_LOGIC;

              Y4 : out STD_LOGIC;
```

```
              Y5 : out STD_LOGIC;

              Y6 : out STD_LOGIC;

              Y7 : out STD_LOGIC);

    End Component;

    Signal EN0, EN1, EN2, EN3, EN4, EN5, EN6,
    EN7 : STD_LOGIC;

begin

    Decoder : Decoder_3_to_8

        Port Map(

            I => En,

            Y0 => EN0,

            Y1 => EN1,

            Y2 => EN2,

            Y3 => EN3,

            Y4 => EN4,

            Y5 => EN5,

            Y6 => EN6,

            Y7 => EN7);

    Reg_4_0 : Reg_4

        Port Map(

            En => EN0,

            Clk => Clk,

            D => "0000",

            Res => Res,

            Q => Q0);

    Reg_4_1 : Reg_4

        Port Map(

            En => EN1,

            Clk => Clk,

            D => D,

            Res => Res,

            Q => Q1);
```

Reg_4_2 : Reg_4

Port Map(

En => EN2,

Clk => Clk,

D => D,

Res => Res,

Q => Q2);

Reg_4_3 : Reg_4

Port Map(

En => EN3,

Clk => Clk,

D => D,

Res => Res,

Q => Q3);

Reg_4_4 : Reg_4

Port Map(

En => EN4,

Clk => Clk,

D => D,

Res => Res,

Q => Q4);

Reg_4_5 : Reg_4

Port Map(

En => EN5,

Clk => Clk,

D => D,

Res => Res,

Q => Q5);

Reg_4_6 : Reg_4

Port Map(

En => EN6,

Clk => Clk,

D => D,

Res => Res,

Q => Q6);

Reg_4_7 : Reg_4

Port Map(

En => EN7,

Clk => Clk,

D => D,

Res => Res,

Q => Q7);

end Behavioral;

MUX 8_1

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Mux_4_8_to_1 is

    Port ( I0 : in STD_LOGIC_VECTOR (3 downto 0);
          I1 : in STD_LOGIC_VECTOR (3 downto 0);
          I2 : in STD_LOGIC_VECTOR (3 downto 0);
          I3 : in STD_LOGIC_VECTOR (3 downto 0);
          I4 : in STD_LOGIC_VECTOR (3 downto 0);
          I5 : in STD_LOGIC_VECTOR (3 downto 0);
          I6 : in STD_LOGIC_VECTOR (3 downto 0);
          I7 : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (2 downto 0);
          Y : out STD_LOGIC_VECTOR (3 downto 0));

end Mux_4_8_to_1;

architecture Behavioral of Mux_4_8_to_1 is

    Component Mux_4_2_to_1

        Port ( I0 : in STD_LOGIC_VECTOR (3 DOWNTO 0);
              I1 : in STD_LOGIC_VECTOR (3 DOWNTO 0);
              S : in STD_LOGIC;
              Y : out STD_LOGIC_VECTOR (3 DOWNTO 0));

    End Component;

    Signal Y0, Y1, Y2, Y3, Y4, Y5 : STD_LOGIC_VECTOR (3 DOWNTO 0);

begin

    Mux_4_2_to_1_0 : Mux_4_2_to_1

        Port Map(

            I0 => I0,

            I1 => I1,

            S => S(0),

            Y => Y0

        );
```

Mux_4_2_to_1_1 : Mux_4_2_to_1

```
Port Map(

    I0 => I2,

    I1 => I3,

    S => S(0),

    Y => Y1

);
```

Mux_4_2_to_1_2 : Mux_4_2_to_1

```
Port Map(

    I0 => I4,

    I1 => I5,

    S => S(0),

    Y => Y2

);
```

Mux_4_2_to_1_3 : Mux_4_2_to_1

```
Port Map(

    I0 => I6,

    I1 => I7,

    S => S(0),

    Y => Y3

);
```

Mux_4_2_to_1_4 : Mux_4_2_to_1

```
Port Map(

    I0 => Y0,

    I1 => Y1,

    S => S(1),

    Y => Y4

);
```

Mux_4_2_to_1_5 : Mux_4_2_to_1

```
Port Map(

    I0 => Y2,

    I1 => Y3,
```

```

S => S(1),
Y => Y5
);

Mux_4_2_to_1_6 : Mux_4_2_to_1
Port Map(
    I0 => Y4,
    I1 => Y5,
    S => S(2),
    Y => Y
);

end Behavioral;

```

MUX 2_1

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if

entity Mux_3_2_to_1 is
    Port ( I0 : in STD_LOGIC_VECTOR (2 DOWNTO 0);
           I1 : in STD_LOGIC_VECTOR (2 DOWNTO 0);
           S : in STD_LOGIC;
           Y : out STD_LOGIC_VECTOR (2 DOWNTO 0));
end Mux_3_2_to_1;

architecture Behavioral of Mux_3_2_to_1 is

Component Mux_2_to_1
    Port ( I0 : in STD_LOGIC;
           I1 : in STD_LOGIC;
           S : in STD_LOGIC;
           Y : out STD_LOGIC);
End Component;

begin

Mux_2_to_1_0: Mux_2_to_1
    Port Map(
        I0 => I0(0),
        I1 => I1(0),
        S => S,
        Y => Y(0)
    );

```

Mux_2_to_1_1: Mux_2_to_1

Port Map(

I0 => I0(1),

I1 => I1(1),

S => S,

Y => Y(1)

);

Mux_2_to_1_2: Mux_2_to_1

Port Map(

I0 => I0(2),

I1 => I1(2),

S => S,

Y => Y(2)

);

end Behavioral;

PROGRAM COUNTER

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Program_Counter is

Port (D : in STD_LOGIC_VECTOR (2 downto 0);

Clk : in STD_LOGIC;

Res : in STD_LOGIC;

Q : out STD_LOGIC_VECTOR (2 downto 0));

end Program_Counter;

architecture Behavioral of Program_Counter is

Component D_FF

Port (D : in STD_LOGIC;

Clk : in STD_LOGIC;

Res : in STD_LOGIC;

Q : out STD_LOGIC);

End Component;

begin

D_FF_0 : D_FF

Port Map(

D => D(0),

Clk => Clk,

Res => Res,

Q => Q(0)

);

D_FF_1 : D_FF

Port Map(


```

D => D(1),
Clk => Clk,
Res => Res,
Q => Q(1)
);

D_FF_2 : D_FF
Port Map(
D => D(2),
Clk => Clk,
Res => Res,
Q => Q(2)
);

end Behavioral;

```

4 BIT ADD SUB UNIT

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Add_Sub_4 is
Port ( Control : in STD_LOGIC;
A : in STD_LOGIC_VECTOR (3 downto 0);
B : in STD_LOGIC_VECTOR (3 downto 0);
S : out STD_LOGIC_VECTOR (3 downto 0);
Overflow : out STD_LOGIC;
Zero : out STD_LOGIC);
end Add_Sub_4;

architecture Behavioral of Add_Sub_4 is
Component RCA_4
Port (
A, B : in STD_LOGIC_VECTOR (3 downto 0);
C_in : in STD_LOGIC;
S : out STD_LOGIC_VECTOR (3 downto 0);
C_out : out STD_LOGIC;
Overflow : out STD_LOGIC
);
End Component;

signal B_new, S_out : STD_LOGIC_VECTOR (3
downto 0);
signal C_out : STD_LOGIC;

begin
B_new(0) <= Control XOR B(0);
B_new(1) <= Control XOR B(1);
B_new(2) <= Control XOR B(2);
B_new(3) <= Control XOR B(3);

```

RCA : RCA_4

Port Map(

A => A,

B => B_new,

C_in => Control,

S => S_out,

C_out => C_out,

Overflow => Overflow

);

Zero <= NOT((C_out) OR S_out(0) OR S_out(1) OR
S_out(2) OR S_out(3));

S <= S_out;

end Behavioral;

3 BIT ADDER

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Adder_3 is

Port (

A : in STD_LOGIC_VECTOR (2 downto 0);

S : out STD_LOGIC_VECTOR (2 downto 0)

);

end Adder_3;

architecture Behavioral of Adder_3 is

Component FA

Port (

A, B, C_in : in std_logic;

S, C_out : out std_logic

);

End Component;

Signal FA0_C, FA1_C, FA2_C : std_logic;

begin

FA_0 : FA

Port Map(

A => A(0),

B => '0',

C_in => '1',

S => S(0),

C_out => FA0_C

);

FA_1 : FA

Port Map(

A => A(1),

B => '0',

C in => FA0_C,

```

        S => S(1),
        C_out => FA1_C
    );

FA_2 : FA
    Port Map(
        A => A(2),
        B => '0',
        C_in => FA1_C,
        S => S(2),
        C_out => FA2_C
    );

end Behavioral;

```

PROGRAM ROM

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all;

entity Program_Rom is

    Port ( memory_select : in STD_LOGIC_VECTOR (2
downto 0);

        instruction_bus : out STD_LOGIC_VECTOR (11
downto 0));

end Program_Rom;

architecture Behavioral of Program_Rom is

    type rom_type is array (0 to 7) of std_logic_vector(11
downto 0);

    signal program_rom : rom_type := (

        "100010000001",  --10 001 000 0001  MOVI R1,1
        "100100000010",  --10 010 000 0010  MOVI R2,2
        "101110000011",  --10 111 000 0011  MOVI R7,3
        "001110100000",  --00 111 010 0000  ADD R7,R2
        "001110010000",  --00 111 001 0000  ADD R7,R1
        "110000000111",  --11 000 0000 111  JZR R0,7
        "000000000000",  --00 000 000 0000  ADD R0,R0
        "110000000101"   --11 000 0000 101  JZR R0,5

    );

    begin

        instruction_bus <=
        program_rom(to_integer(unsigned(memory_select)))
        ;

    end Behavioral;

```

LUT_16 7 SEG

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity LUT_16_7 is

    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));

end LUT_16_7;

architecture Behavioral of LUT_16_7 is

    type rom_type is array (0 to 15) of std_logic_vector(6
downto 0);

    signal sevenSegment_ROM : rom_type := (

        "1000000", -- 0
        "1111001", -- 1
        "0100100", -- 2
        "0110000", -- 3
        "0011001", -- 4
        "0010010", -- 5
        "0000010", -- 6
        "1111000", -- 7
        "0000000", -- 8
        "0010000", -- 9
        "0001000", -- a
        "0000011", -- b
        "1000110", -- c
        "0100001", -- d
        "0000110", -- e
        "0001110" -- f
    );

    begin

    data <=
    sevenSegment_ROM(to_integer(unsigned(address)));

end Behavioral;
```

REGISTER

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Reg is

    Port ( En : in STD_LOGIC;

          Clk : in STD_LOGIC;

          D : in STD_LOGIC;

          Res : in STD_LOGIC;

          Q : out STD_LOGIC := '0');

end Reg;

architecture Behavioral of Reg is

begin

    process (Clk) begin

        if (Res = '1') then

            Q <= '0';

        end if;

        if (En = '1') then

            if (rising_edge(Clk)) then

                Q <= D;

            end if;

        end if;

    end process;

end Behavioral;
```

REG_4

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg_4 is
    Port ( En : in STD_LOGIC;
          Clk : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR (3 downto 0);
          Res : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0):=
"0000");
end Reg_4;
```

architecture Behavioral of Reg_4 is

Component Reg

```
Port ( En : in STD_LOGIC;
      Clk : in STD_LOGIC;
      D : in STD_LOGIC;
      Res : in STD_LOGIC;
      Q : out STD_LOGIC := '0');
```

End Component;

begin

Reg_0 : Reg

```
Port Map(
    En => En,
    Clk => Clk,
    D => D(0),
    Res => Res,
    Q => Q(0)
);
```

Reg_1 : Reg

Port Map(

```
    En => En,
    Clk => Clk,
    D => D(1),
    Res => Res,
    Q => Q(1)
);
```

Reg_2 : Reg

```
Port Map(
    En => En,
    Clk => Clk,
    D => D(2),
    Res => Res,
    Q => Q(2)
);
```

Reg_3 : Reg

```
Port Map(
    En => En,
    Clk => Clk,
    D => D(3),
    Res => Res,
    Q => Q(3)
);
```

end Behavioral;

DECODER 3_8

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_to_8 is

Port (I : in STD_LOGIC_VECTOR (2 downto 0);

Y0 : out STD_LOGIC;

Y1 : out STD_LOGIC;

Y2 : out STD_LOGIC;

Y3 : out STD_LOGIC;

Y4 : out STD_LOGIC;

Y5 : out STD_LOGIC;

Y6 : out STD_LOGIC;

Y7 : out STD_LOGIC);

end Decoder_3_to_8;

architecture Behavioral of Decoder_3_to_8 is

Signal I0P, I1P, I2P : STD_LOGIC;

Signal A0, A1, A2, A3 : STD_LOGIC;

begin

I0P <= NOT(I(0));

I1P <= NOT(I(1));

I2P <= NOT(I(2));

A0 <= I1P AND I2P;

A1 <= I(1) AND I2P;

A2 <= I1P AND I(2);

A3 <= I(1) AND I(2);

Y0 <= A0 AND I0P;

Y1 <= A0 AND I(0);

Y2 <= A1 AND I0P;

Y3 <= A1 AND I(0);

Y4 <= A2 AND I0P;

Y5 <= A2 AND I(0);

Y6 <= A3 AND I0P;

Y7 <= A3 AND I(0);

end Behavioral;

NANO PROCESSOR

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Nano_Processor is

Port (Clk : in STD_LOGIC;

Reset : in STD_LOGIC;

Overflow : out STD_LOGIC;

Zero : out STD_LOGIC;

Answer: out STD_LOGIC_VECTOR(3 downto 0));

end Nano_Processor;

architecture Behavioral of Nano_Processor is

component Instruction_Decoder

Port (Ins : in STD_LOGIC_VECTOR (11 downto 0);

RegJmp : in STD_LOGIC_VECTOR (3 downto 0);

RegEn : out STD_LOGIC_VECTOR (2 downto 0);

LoadSel : out STD_LOGIC;

ImVal : out STD_LOGIC_VECTOR (3 downto 0);

RegSel1 : out STD_LOGIC_VECTOR (2 downto 0);

RegSel2 : out STD_LOGIC_VECTOR (2 downto 0);

AddSubSel : out STD_LOGIC;

Jmp : out STD_LOGIC;

AddressJmp : out STD_LOGIC_VECTOR (2 downto 0));

end component;

component Reg_Bank

Port (En : in STD_LOGIC_VECTOR (2 downto 0);

Clk : in STD_LOGIC;

Res : in STD_LOGIC;

D : in STD_LOGIC_VECTOR (3 downto 0);

Q0 : out STD_LOGIC_VECTOR (3 downto 0);

Q1 : out STD_LOGIC_VECTOR (3 downto 0);

Q2 : out STD_LOGIC_VECTOR (3 downto 0);

Q3 : out STD_LOGIC_VECTOR (3 downto 0);

Q4 : out STD_LOGIC_VECTOR (3 downto 0);

Q5 : out STD_LOGIC_VECTOR (3 downto 0);

Q6 : out STD_LOGIC_VECTOR (3 downto 0);

Q7 : out STD_LOGIC_VECTOR (3 downto 0));

end component;

component Mux_4_8_to_1

Port (I0 : in STD_LOGIC_VECTOR (3 downto 0);

I1 : in STD_LOGIC_VECTOR (3 downto 0);

I2 : in STD_LOGIC_VECTOR (3 downto 0);

I3 : in STD_LOGIC_VECTOR (3 downto 0);

I4 : in STD_LOGIC_VECTOR (3 downto 0);

I5 : in STD_LOGIC_VECTOR (3 downto 0);

I6 : in STD_LOGIC_VECTOR (3 downto 0);

I7 : in STD_LOGIC_VECTOR (3 downto 0);

S : in STD_LOGIC_VECTOR (2 downto 0);

Y : out STD_LOGIC_VECTOR (3 downto 0));

end component;

component Mux_3_2_to_1

Port (I0 : in STD_LOGIC_VECTOR (2 DOWNTO 0);

I1 : in STD_LOGIC_VECTOR (2 DOWNTO 0);

S : in STD_LOGIC;

Y : out STD_LOGIC_VECTOR (2 DOWNTO 0));

end component;

component Mux_4_2_to_1

Port (I0 : in STD_LOGIC_VECTOR (3 DOWNTO 0);

I1 : in STD_LOGIC_VECTOR (3 DOWNTO 0);

S : in STD_LOGIC;

```

        Y : out STD_LOGIC_VECTOR (3 DOWNTO 0));
end component;

component Program_Counter
    Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
          Clk : in STD_LOGIC;
          Res : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Add_Sub_4
    Port ( Control : in STD_LOGIC;
          A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          S : out STD_LOGIC_VECTOR (3 downto 0);
          Overflow : out STD_LOGIC;
          Zero : out STD_LOGIC);
end component;

component Adder_3
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          S : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Program_Rom
    Port ( memory_select : in STD_LOGIC_VECTOR (2
downto 0);
          instruction_bus : out STD_LOGIC_VECTOR (11
downto 0));
end component;

component Slow_Clk
    Port ( Clk_in : in STD_LOGIC;

```

```

          Clk_out : out STD_LOGIC);
end component;

signal I : STD_LOGIC_VECTOR (11 downto 0);
signal M, mux1_out, mux2_out, add_sub_out,
immediate_value, D0,D1, D2,D3,D4,D5,D6,D7 :
STD_LOGIC_VECTOR (3 downto 0);

signal register_enable, register_select_1, register_select_2,
address_to_jump, adder_out : STD_LOGIC_VECTOR (2
downto 0);

signal clock_out, load_select, jump_flag, add_sub_select :
std_logic;

signal memory_select, pc_in : STD_LOGIC_VECTOR (2
downto 0):= "000";

begin

--  pc_in <= "000";
--  memory_select <= "000";
--  adder_out <= "000";

slow_clock_0 : Slow_Clk
    port map ( Clk_in => Clk,
              Clk_out => clock_out);

Instruction_Decoder_0 : Instruction_Decoder
    Port map ( Ins => I,
              RegJmp => mux1_out,
              RegEn => register_enable,
              LoadSel => load_select,
              ImVal => immediate_value,
              RegSel1 => register_select_1,
              RegSel2 => register_select_2,

```



```

    Jmp => jump_flag,
    AddSubSel => add_sub_select,
    AddressJmp => address_to_jump);

```

Reg_Bank_0 :Reg_Bank

```

    Port map ( En => register_enable,
               Clk => clock_out,
               Res => reset,
               D => M,
               Q0 => D0,
               Q1 => D1,
               Q2 => D2,
               Q3 => D3,
               Q4 => D4,
               Q5 => D5,
               Q6 => D6,
               Q7 => D7);

```

Mux_4_8_to_1_1 :Mux_4_8_to_1

```

    Port map ( I0 => D0,
               I1 => D1,
               I2 => D2,
               I3 => D3,
               I4 => D4,
               I5 => D5,
               I6 => D6,
               I7 => D7,
               S => register_select_1,
               Y => mux1_out);

```

Mux_4_8_to_1_2 :Mux_4_8_to_1

```

    Port map ( I0 => D0,

```

```

    I1 => D1,
    I2 => D2,
    I3 => D3,
    I4 => D4,
    I5 => D5,
    I6 => D6,
    I7 => D7,
    S => register_select_2,
    Y => mux2_out);

```

Mux_3_2_to_1_0 :Mux_3_2_to_1

```

    Port map ( I0 => adder_out,
               I1 => address_to_jump,
               S => jump_flag,
               Y => pc_in);

```

Mux_4_2_to_1_0 :Mux_4_2_to_1

```

    Port map ( I0 => add_sub_out,
               I1 => immediate_value,
               S => load_select,
               Y => M);

```

Program_Counter_0 :Program_Counter

```

    Port map ( D => pc_in,
               Clk => clock_out,
               Res => reset,
               Q => memory_select);

```

Add_Sub_4_0 :Add_Sub_4

```

    Port map ( Control => add_sub_select,
               A => mux2_out,
               B => mux1_out,

```

```
S => add_sub_out,  
Overflow => Overflow,  
Zero => Zero);
```

```
Adder_3_0 :Adder_3
```

```
Port map ( A => memory_select,  
          S => adder_out);
```

```
ProgramROM_0 :Program_Rom
```


```
Port map ( memory_select => memory_select,  
          instruction_bus => I);
```

```
Answer <= D7;
```


```
end Behavioral;
```

TIMING DIAGRAMS


1. SLOW CLOCK

 


2. INSTRUCTION DECODER

 


3. REGISTER BANK

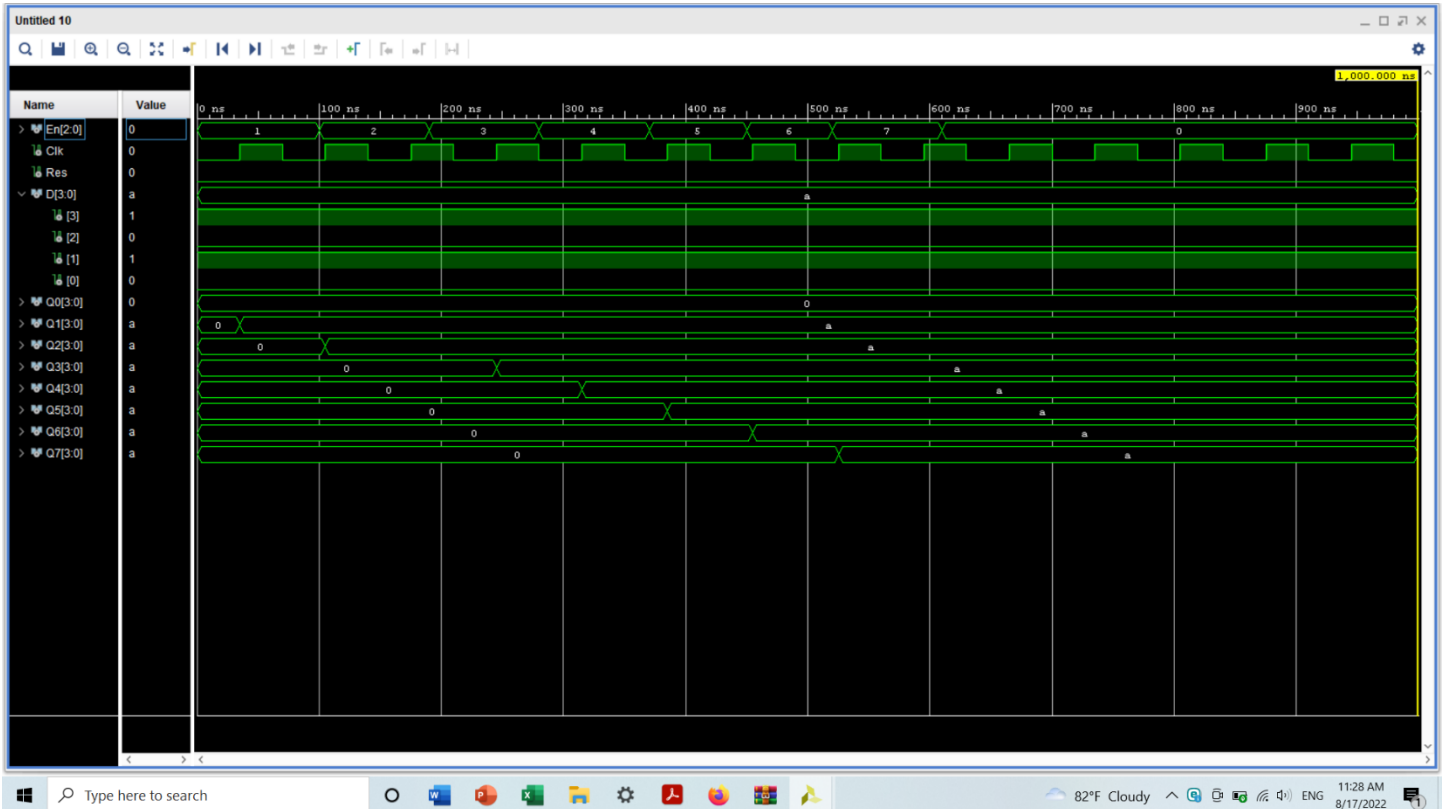


4. MUX 8_1

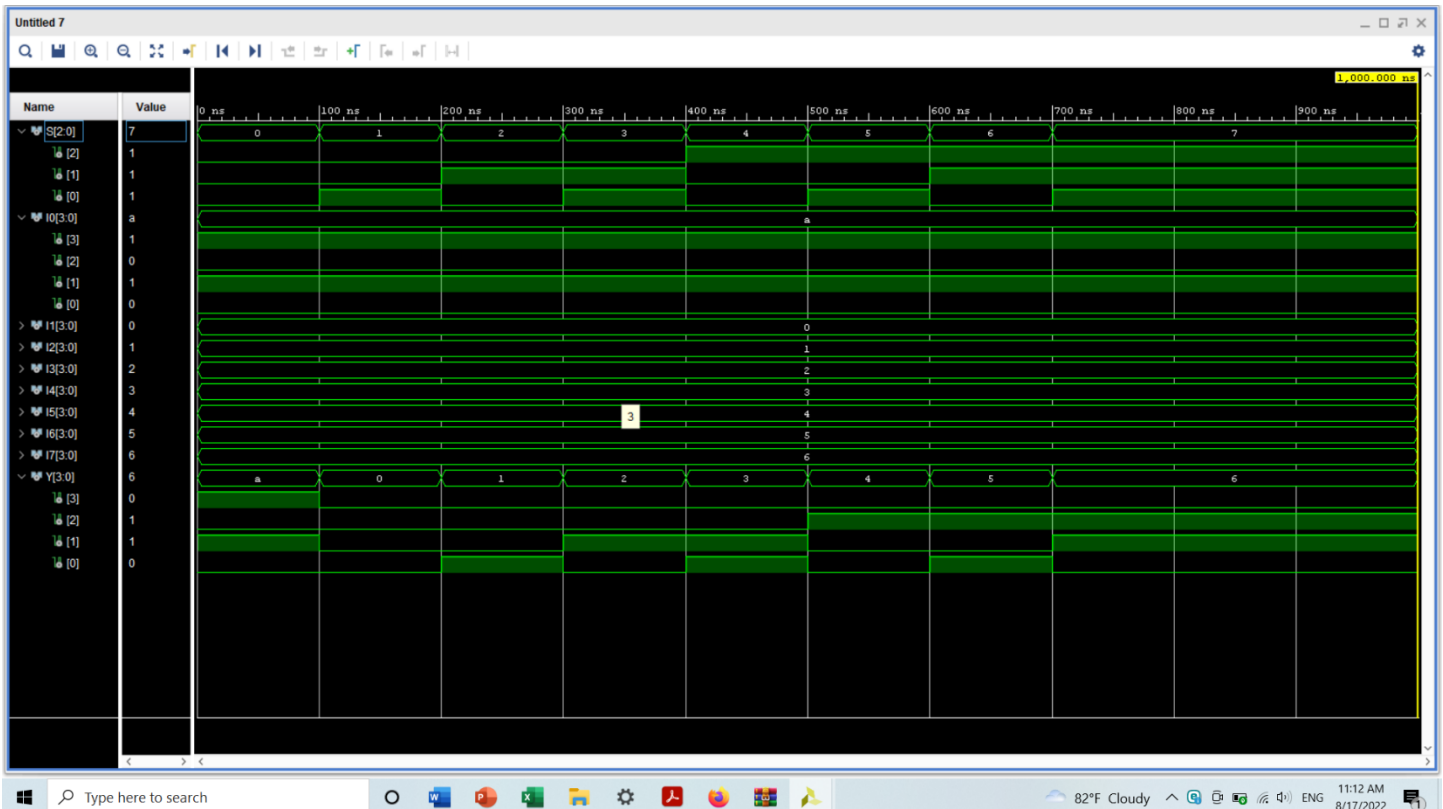


5. MUX 2_1

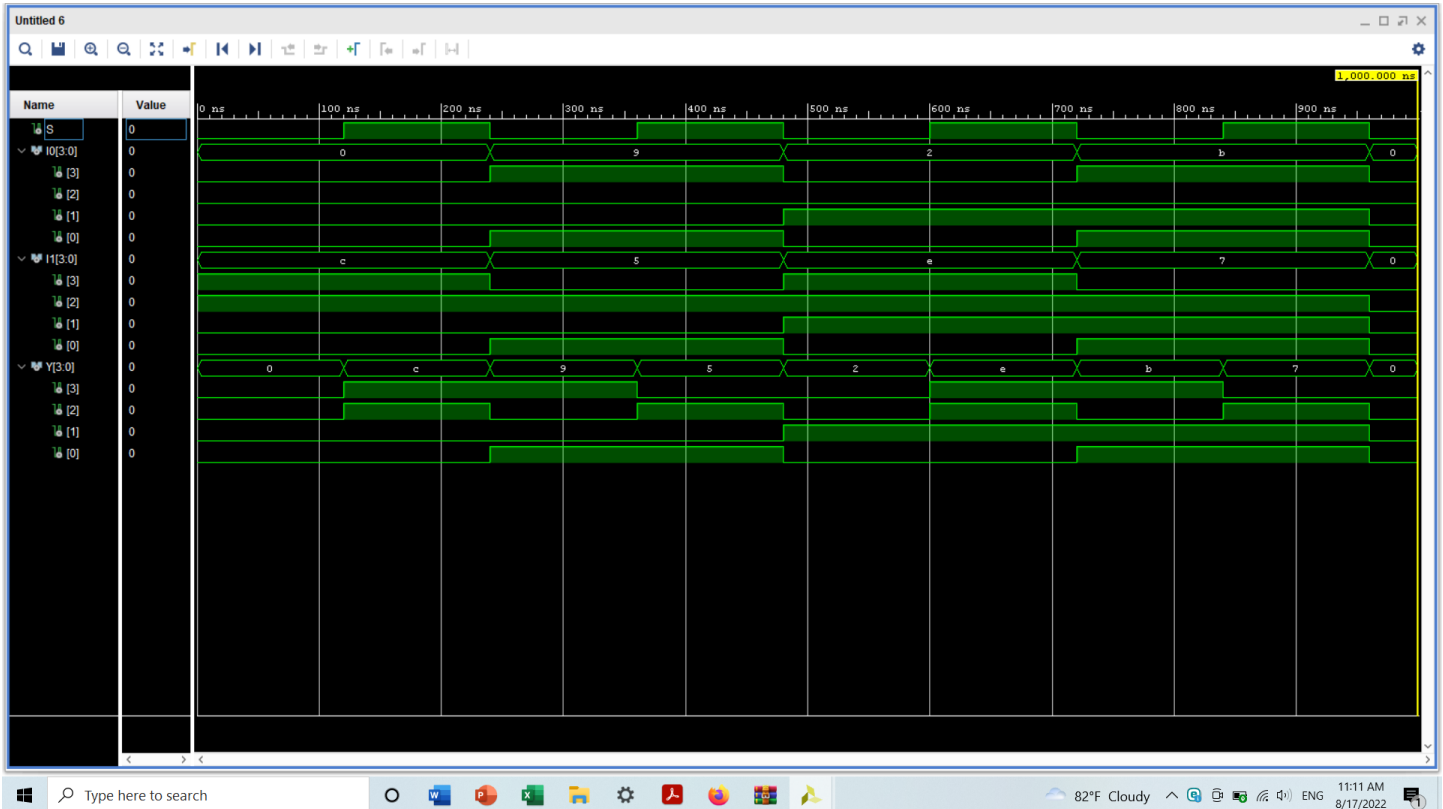


6. PROGRAM COUNTER

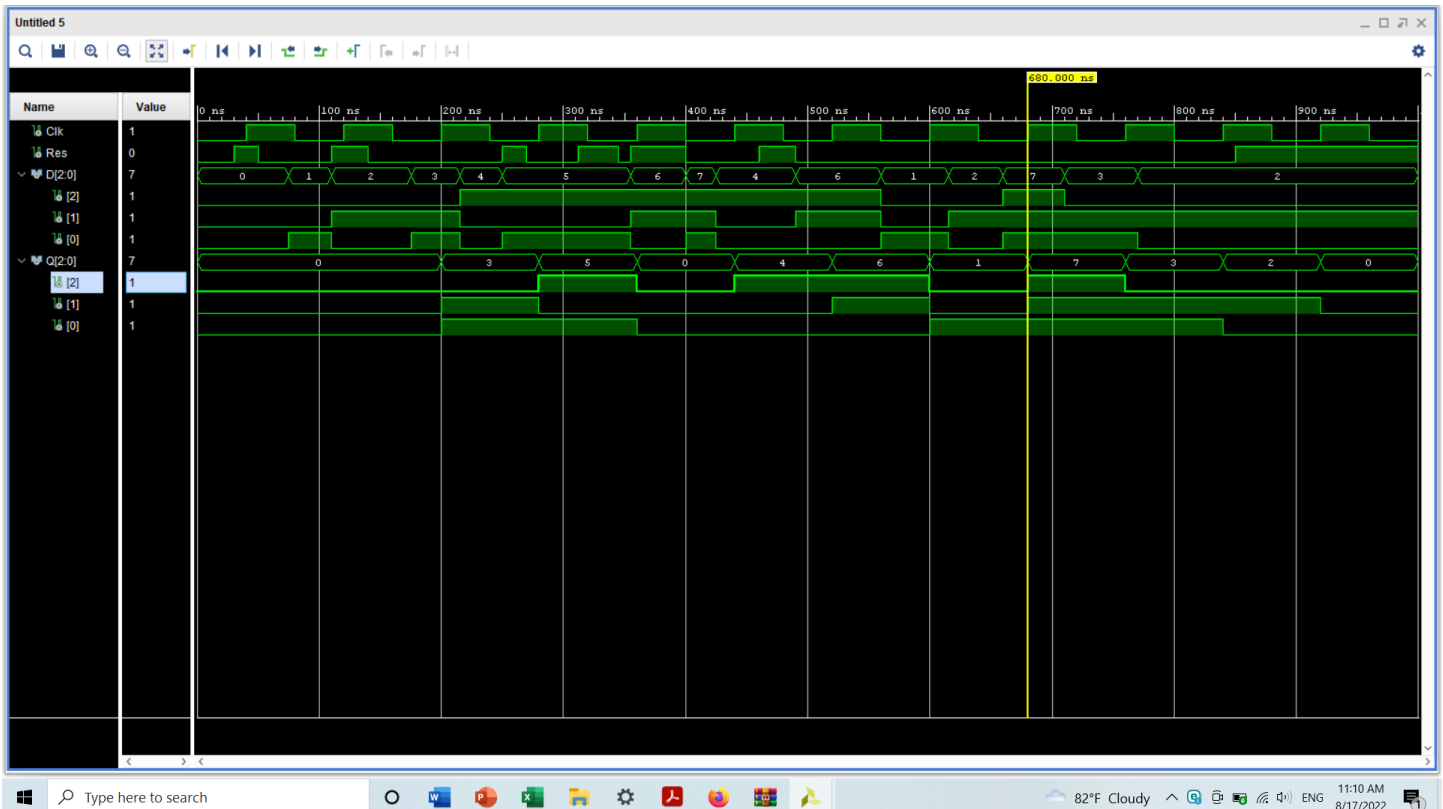

7. 4 BIT ADD AND SUB UNIT

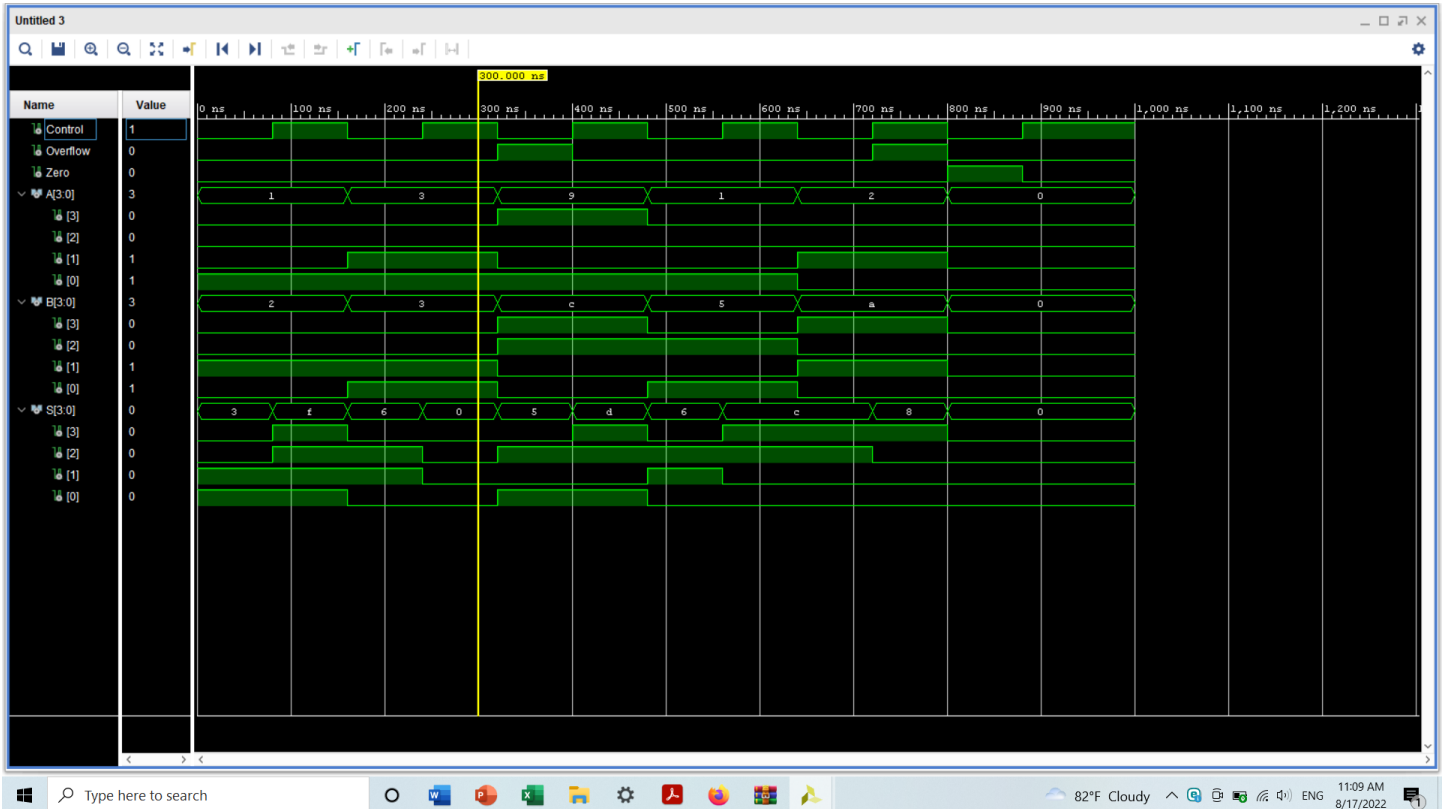


8. 3 BIT ADDER

 


9. PROGRAM ROM




10. REGISTER

 


11. REG_4

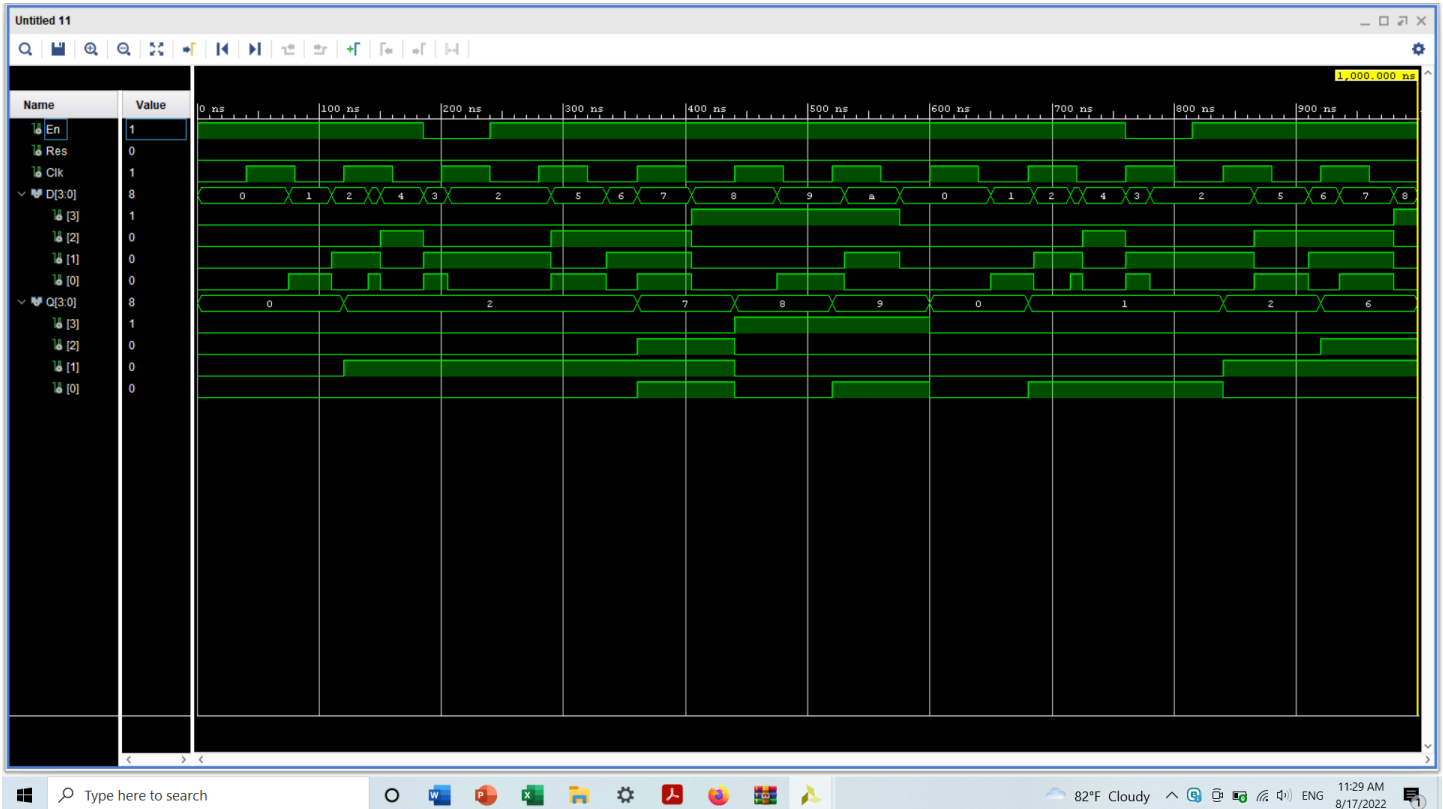

12. DECODER 3_8

 

13. NANO PROCESSOR 7 SEG

 

CONCLUSIONS:

- As the nano processor only understands binary values, we need to hardcode assembly instructions as binary values.
- Using the 4-bit arithmetic unit we can do arithmetic operations with input signals of 4 bits.
- To run a nano processor a clock signal is essential.
- Usage of buses simplify the design.
- Slice logic and primitive tables in synthesis report can be used to observe the optimizations done to the nano processor.
- With the integration of previously created components and using them in hierarchical order made the development process less complicated and reusable.
- In a project like this, as the components are getting complicated, it is easier to distribute and delegate the workload.
- Program counter points to the next suitable instruction set.
- Register bank is used to store the 4-bit binary values in each register with help of d flipflops.
- Instruction decoder act as the main controlling hub in the nano processor which decode the binary instruction and send suitable input signals for suitable components.
- 4-bit Adder/Subtractor can add and subtract 2 4-bit binary inputs and give the output with overflow and zero signals.
- To select an input from a set of inputs, we mainly used different multiplexers.

OPTIMIZATIONS:

Instead of using previously built components, we built 3 to 8 decoders, multiplexers, and 4 bit adder subtractors from ground up that resulted in 52 slice LUTs and 53 slice registers as flip flops.

CONTRIBUTION FROM THE TEAM:

A.A.A. Jasmin 200238N	<ul style="list-style-type: none">• Instruction Decoder• Multiplexers• Nano processor assembly• Simulation of multiplexers, instruction decoder, nano processor
K.G.T.R. Kumaratunga 200327L	<ul style="list-style-type: none">• 4-bit adder subtractor• Simulation of 4-bit adder subtractor, register bank, 3-to-8 decoder
K.V.R. Kurukulasooriya 200332X	<ul style="list-style-type: none">• Program rom• Simulation of program rom• Documentation
G.S.D. Kuruppu 200333C	<ul style="list-style-type: none">• 3-bit program counter• 3-bit adder• Simulation of 3-bit program counter, 3-bit adder
G.M.P. Silva 200605M	<ul style="list-style-type: none">• Register bank• 3-to-8 decoder• Nano processor 7 segment integration